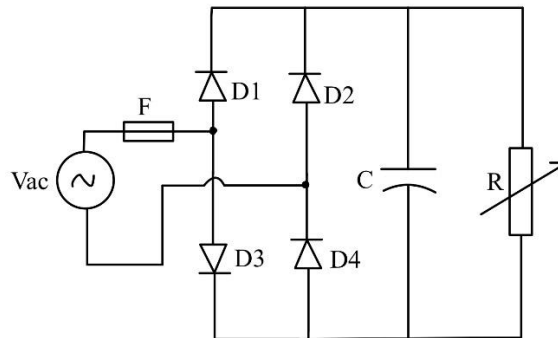


*Question 1:*

*While connecting the diodes of a full bridge rectifier, the Power electronics engineer made a mistake and connected one of the diodes with wrong polarity as shown in the figure below. The circuit was then connected to 230V AC supply, through a semiconductor fuse. Which of the following statements are FALSE?*

*(Assume the forward drop of diode is 0 V)*



1. *Circuit will work properly during positive half cycle and no current will flow during negative half cycle.*
2. *The Semiconductor fuse used in the circuit would blow up immediately.*
3. *The capacitor will blow up if fuse is not used.*
4. *The load resistor will blow up if fuse is not used.*
5. *Diode  $D1$  and  $D4$  will be damaged if fuse is not used.*
6. *Diode  $D2$  will not be damaged.*
7. *Diode  $D3$  and  $D4$  will be damaged if fuse is not used.*

- a) 1,3,4,6
- b) 2,3,5,6
- c) 1,3,4,5
- d) 1,2,6,7

**Solution:** Correct option is (c)

Due to the wrong connection made, during positive half cycle,  $D3$  and  $D4$  will be forward biased and thus the AC supply is shorted and huge currents will flow and the semiconductor fuse will blow up. Semiconductor fuses are extremely fast and can act in few milliseconds or even less than a millisecond. So, if the fuse is used, the diodes  $D3$  and  $D4$  will be protected. Otherwise, they will blow up. In the negative half cycle, there is no path for current to flow. Hence  $D2$ , Output Capacitor  $C$  and Load Resistor  $R$  will not blow up whether fuse is used or not.

$D1$  is forward biased during positive half cycle, but no current will flow through  $D1$  and through  $R||C$ , because the supply has a dead short through  $D3$  and  $D4$  and all the currents will flow through  $D3$  and  $D4$ . Therefore,  $D1$  will not be damaged.

### Question 2:

In a particular rectifier circuit, the AC supply (230V, 50Hz) is turned ON exactly at the zero crossing (using a Zero Crossing Detection Circuit). Based on the load conditions, the Power Electronics Engineer calculated the amplitude of the inrush current during the first cycle when the supply is turned ON. The amplitude came out to be 75A. Also, his circuit will be operating in an ambient temperature of 37.5°C. The engineer checks through the datasheet of 1N4007 to see whether it can handle 75A of surge current at the starting. He finds out that the maximum tolerable surge current of 1N4007 diode at 37.5°C is \_\_\_\_\_.

(The datasheet is attached. The student is advised to go through the data sheet thoroughly and find the value of surge current. Assume for simplicity that the inrush current pulse is square pulse)

( <https://www.vishay.com/docs/88503/1n4001.pdf> )

Solution: **Range (28-30)**

Since the source is turned at zero crossing, for the source to reach the peak, it will take 5ms for the source to reach the peak value. So, the inrush current pulse will flow for 5ms. Even though it is not exactly a square, as allowed in the question, we will take it as a square.

This inrush current happens only in the first cycle when the supply is turned ON. It doesn't repeat for the consecutive cycles and therefore we have to look at the **non-repetitive peak forward surge current** value mentioned in the datasheet. Looking at the tables, we get

MAXIMUM RATINGS (T <sub>A</sub> = 25 °C unless otherwise noted)									
PARAMETER	SYMBOL	1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	UNIT
Maximum repetitive peak reverse voltage	V <sub>RRM</sub>	50	100	200	400	600	800	1000	V
Maximum RMS voltage	V <sub>RMS</sub>	35	70	140	280	420	560	700	V
Maximum DC blocking voltage	V <sub>DC</sub>	50	100	200	400	600	800	1000	V
Maximum average forward rectified current 0.375" (9.5 mm) lead length at T <sub>A</sub> = 75 °C	I <sub>F(AV)</sub>	1.0							A
Peak forward surge current 8.3 ms single half sine-wave superimposed on rated load	I <sub>FSM</sub>	30							A
Non-repetitive peak forward surge current square waveform T <sub>A</sub> = 25 °C (Fig. 3)	t <sub>p</sub> = 1 ms	45							A
	t <sub>p</sub> = 2 ms	35							
	t <sub>p</sub> = 5 ms	30							
Maximum full load reverse current, full cycle average 0.375" (9.5 mm) lead length T <sub>L</sub> = 75 °C	I <sub>R(AV)</sub>	30							μA
Rating for fusing (t < 8.3 ms)	P <sub>T</sub> (†)	3.7							A <sup>2</sup> s
Operating junction and storage temperature range	T <sub>J</sub> , T <sub>STG</sub>	-50 to +150							°C

The tables provide the value at 25°C. In order to get the exact value at 37.5°C, we need to look at the characteristics. We can see from the characteristics, that the value of surge current is nearly 29 A at 37.5°C (marked in RED).


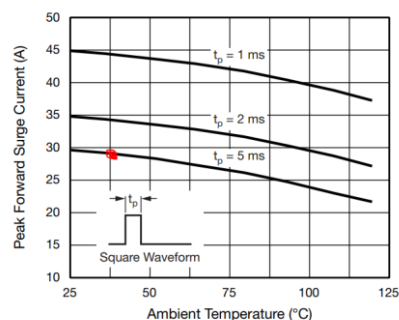


Fig. 3 - Non-Repetitive Peak Forward Surge Current

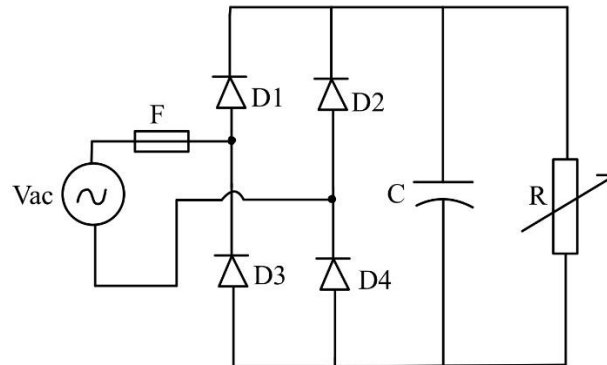*Question 3:*

*In the diode bridge rectifier circuit given below, which of the following statements are true, if diode D2 is damaged and acts as OPEN for the entire time of operation.*




1. The Capacitor voltage ripple for a given load current will be lesser than the circuit in which D2 is working properly.
2. If the load current is extremely small, the output voltage will appear to be approximately the same whether D2 is working properly or not.
3. If the load current is very large, the output voltage can also come down to zero, before the positive half of the next cycle.

- a) 1,2,3
- b) 2,3
- c) 1,3
- d) None are correct

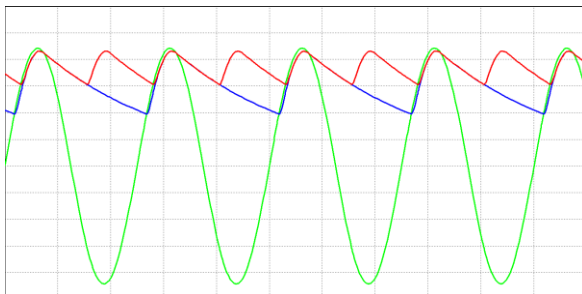**Solution: (b)**

When D2 is open, no current will flow during the negative half cycle and therefore the capacitor will discharge for a longer time and thus the capacitor voltage ripple will be larger.



The green waveform is the input voltage. The red waveform is the output voltage when D2 is working properly. The blue waveform is the output voltage when D2 is OPEN.

When the load current is very large, the capacitor will discharge quickly and be at 0V.

When the load current is very small, the capacitor will discharge very slowly and thus the output voltage ripple will be less and the voltage waveform will look alike in both the cases.

*Question 4:*

*While selecting the capacitor for the diode full bridge rectifier, the Power Electronics Engineer must look into several parameters to decide the capacitor and one of them is the **maximum voltage across the capacitor**. The engineer must design this rectifier for a particular country where the standard AC voltage is 110Vrms ,60Hz. There can be a fluctuation of 40% around the standard value. Considering the fluctuation in supply voltage, and giving a margin of 20% on top of the fluctuations, what is the nearest voltage rating of the capacitor that the engineer arrives at:*

- a) 218 V
- b) 154 V
- c) 282V
- d) 262 V

**Solution: (D)**

*Standard average RMS voltage = 110 Vrms*

$$\text{Maximum RMS voltage of the supply} = 110 + 110 \times \frac{40}{100} = 154 \text{ Vrms}$$

$$\text{The peak voltage for the maximum condition} = V_{rms} \times \sqrt{2} = 154 \times 1.414 = 217.756 \text{ V}$$

$$\text{Adding 20\% margin to this we get } V_m = 217.756 \times 1.2 = 261.307 \approx 262 \text{ V}$$

The engineer will obviously not find a capacitor of this exact voltage rating, but he must choose a voltage rating for the capacitor very near to 262 V that is available in the market.

**Question 5:**

For a particular application, after the circuit designer did all the necessary circuit analysis he came up with the following values for the capacitor

$$C = 215 \mu F ; V_c = 320V ; I_{CRMS} = 1.5A$$

A datasheet of a series of capacitors were handed to him. All the capacitors in this datasheet are rated at 500V. So the voltage aspect is taken care of. **He has to make sure that at all times, the capacitance should be 215uF.** The designer goes through the datasheet and write the code for the capacitor that he will choose finally is \_\_\_\_\_.

(The datasheet of the Electrolytic capacitor is attached. The student is advised to go through the datasheet thoroughly and find the code of the capacitor required for the above application.

( [https://www.nichicon.co.jp/english/series\\_items/catalog\\_pdf/e-lgc.pdf](https://www.nichicon.co.jp/english/series_items/catalog_pdf/e-lgc.pdf) )

**Solution: LGC2H271MELA50**

Voltage is 500V for all the capacitors. Therefore, we need not worry about voltage as it is way beyond 320V.

Now the capacitance designed is 215uF. We will be tempted to choose from the 220uF category. But the datasheet states that the capacitance has a tolerance of 20%.

Capacitance Tolerance	±20% at 120Hz, 20°C
-----------------------	---------------------

This implies that in the worst-case scenario, the capacitance will be

$$220 - 220 * \frac{20}{100} = 176 \mu F$$

Therefore, the designer will choose the 270uF category. Considering the tolerance, the minimum capacitance will be:

$$270 - 270 * \frac{20}{100} = 216 \mu F$$


Now within this section, there are 4 available capacitors, and they differ mainly in the maximum RMS value permissible.

270	22 × 60	1620	1.10	LGC2H271MELZ60
	25 × 50	1600	1.10	LGC2H271MELA50
	30 × 35	1480	1.10	LGC2H271MELB35
	35 × 30	1430	1.10	LGC2H271MELC30

For our application, the maximum RMS value is 1.5 A. Therefore, the designer will choose the capacitor with rms current higher than that which is 1.6 A which corresponds to LGC2H271MELA50.

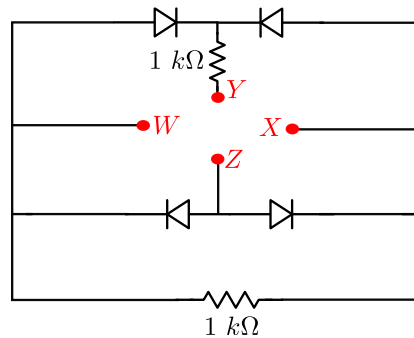**Question 6:**


A voltage  $100 \sin(\omega t)$  is applied across YZ. Assuming diodes to be ideal, the voltages measured across WX (in volts) is



- (a)  $\sin(\omega t)$
- (b)  $(\sin(\omega t) + |\sin(\omega t)|)/2$
- (c)  $(\sin(\omega t) - |\sin(\omega t)|)/2$
- (d) 0 for all  $t$


Solution: Correct option is (d)

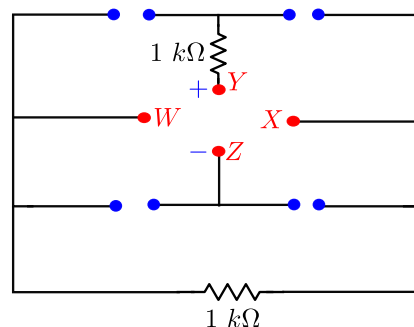During the positive half cycle the circuit becomes:



Thus, the voltage across 'WX' during the positive half cycle is 0 V.

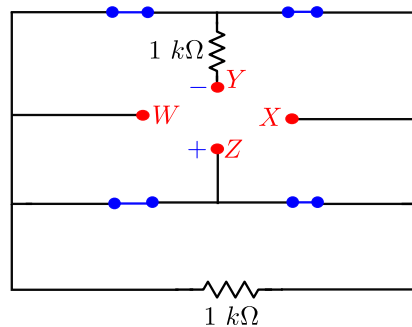
During the negative half cycle the circuit becomes:



Thus, the voltage across 'WX' during the negative half cycle is 0 V.

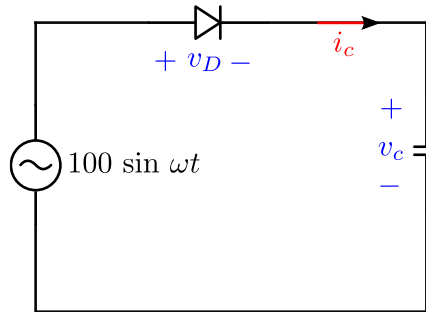**Question 7: Numerical type**

In the circuit shown below find the rms value of the voltage (in volts) across the diode in steady state.




**Solution: Answer range (121-123)**

In the positive half cycle, the diode gets forward biased and starts conducting for the period

$0 \leq \omega t \leq \frac{\pi}{2}$ . Thus, during this period

$$v_c = 100 \sin(\omega t)$$

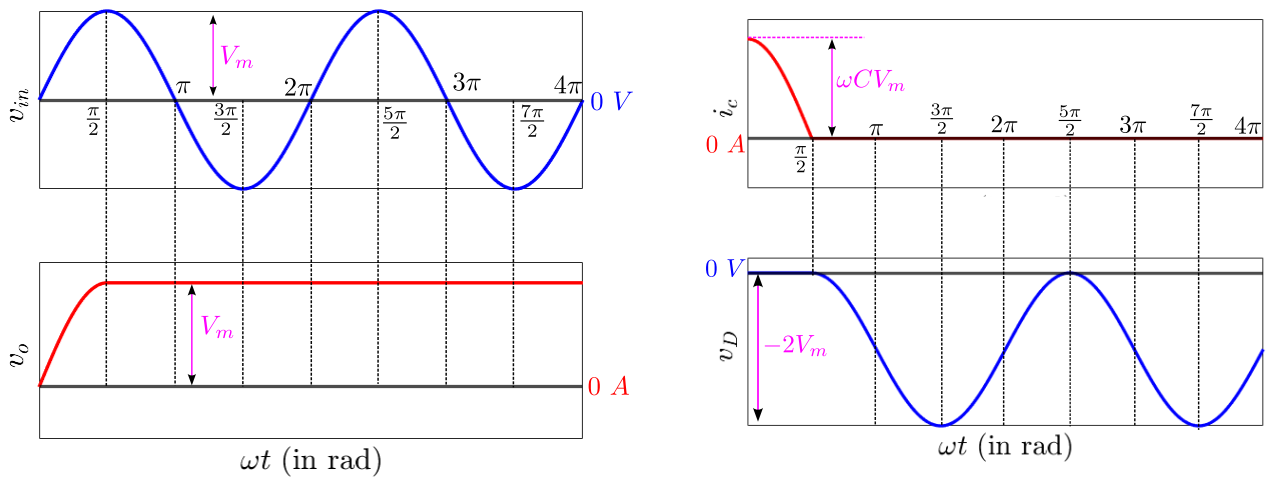At  $\omega t = \frac{\pi}{2}$ , the voltage across the capacitors reaches its maximum value  $V_m = 100 \text{ V}$ . Thus, the diode gets reverse biased for  $\omega t > \frac{\pi}{2}$  and the current through the diode,  $i_c$  stays put at 0 A. The corresponding waveforms are illustrated in the figures below:



Therefore, at steady state i.e. for  $\omega t > \frac{\pi}{2}$ , the expression for the diode voltage can be written as

$$v_D = V_m(\sin(\omega t) - 1)$$

Thus, from the expression we can conclude that the average value of the  $v_D$  is

$$V_{D,avg} = \langle v_D \rangle_T = \frac{V_m}{2\pi} \int_0^{2\pi} (\sin(\omega t) - 1) d(\omega t) = V_m$$

Rms value of the fundamental component of  $v_D$  is

$$V_{1,rms} = \frac{V_m}{\sqrt{2}}$$


The rms value of the voltage across diode is thus given by

$$V_{D,rms} = \sqrt{V_{D,avg}^2 + V_{1,rms}^2} = \sqrt{\frac{3}{2}} V_m = 122.47 \text{ V}$$




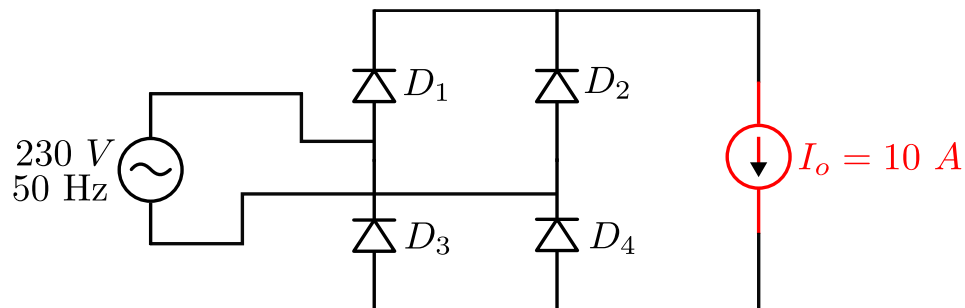**Question 8:**


The figure shows the circuit of a rectifier fed from a 230 V (rms), 50 Hz sinusoidal voltage source. If we want to replace the current source with a resistor so that the rms value of the current supplied by the voltage source remains unchanged, the value of resistance (in  $\Omega$ ) is \_\_\_\_\_ (Assume diodes to be ideal).



**Solution:** Answer range (22.99-23)

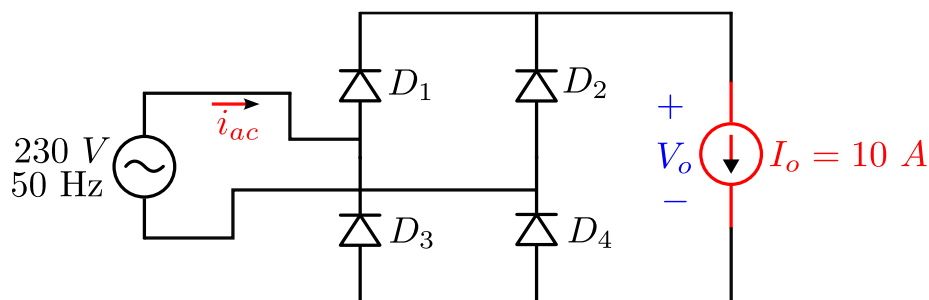

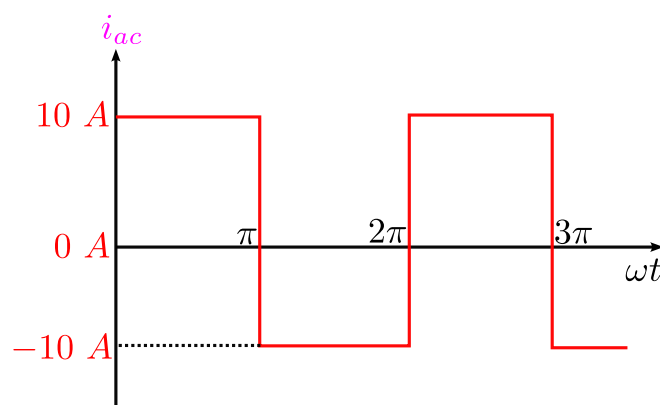
With the current source in the circuit, the waveform of  $i_{ac}$  is illustrated in the figure below



Thus, the rms value of the current,  $i_{ac}$ , supplied by the voltage source is

$$i_{ac,rms} = 10 \text{ A}$$

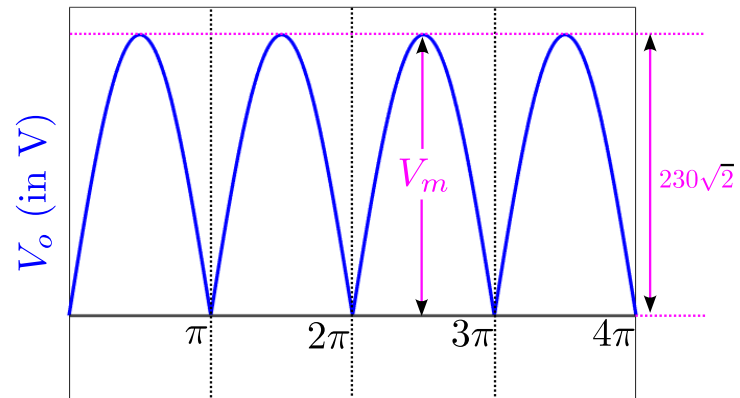The waveform of the output voltage,  $V_o$ , is illustrated in the figure below



The rms value of the output voltage,  $V_o$ , is given by


$$V_{o,rms} = \frac{V_m}{\sqrt{2}} = 230 \text{ V}$$

Now, if we want to replace the current source with a resistive load such that the rms current remains same as  $i_{ac,rms}$ , then the value of the resistive load can be obtained as

$$R_L = \frac{V_{o,rms}}{i_{ac,rms}} = 23 \text{ } \Omega$$

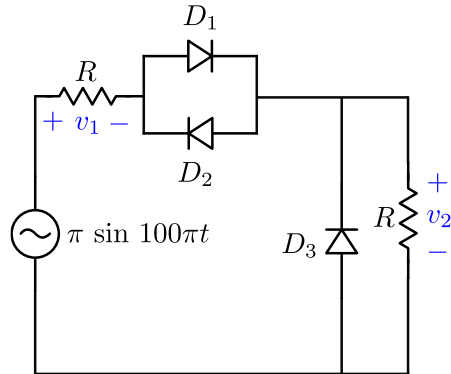**Question 9:**

For the circuit shown below assume the diodes  $D_1$ ,  $D_2$  and  $D_3$  to be ideal.



The dc components of voltages  $v_1$ , and  $v_2$  respectively are

- (a) 0 V and 1 V
- (b) -0.5 V and 0.5 V
- (c) 1 V and 0.5 V
- (d) 1 V and 1 V

Solution: Correct option is (b)

During the positive half cycle,  $D_1$  is forward biased and  $D_2$  and  $D_3$  are reverse biased. Thus, during this period

$$v_1 = v_2 = \frac{\pi}{2} \sin(100\pi t)$$

During the negative half cycle,  $D_1$  is reverse biased and  $D_2$  and  $D_3$  are forward biased. Thus, during this period

$$v_1 = \pi \sin(100\pi t) \quad \text{and} \quad v_2 = 0 \text{ V}$$

Now, we can calculate the average value of  $v_1$  as






$$\langle v_1 \rangle_T = \frac{1}{2\pi} \left[ \int_0^\pi \frac{\pi}{2} \sin(\omega t) d(\omega t) + \int_\pi^{2\pi} \pi \sin(\omega t) d(\omega t) \right] = -\frac{1}{2}$$

Similarly, we can calculate the average value of  $v_2$  as

$$\langle v_2 \rangle_T = \frac{1}{2\pi} \left[ \int_0^\pi \frac{\pi}{2} \sin(\omega t) d(\omega t) \right] = \frac{1}{2}$$

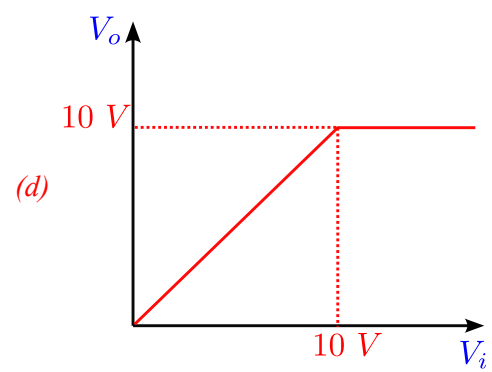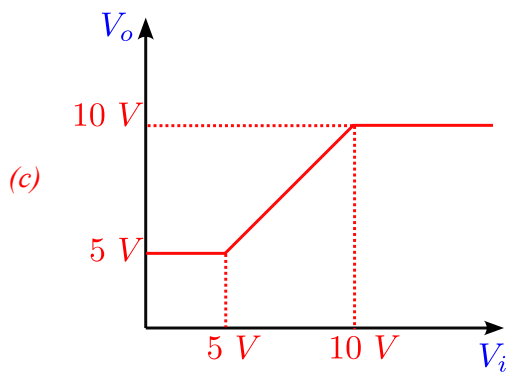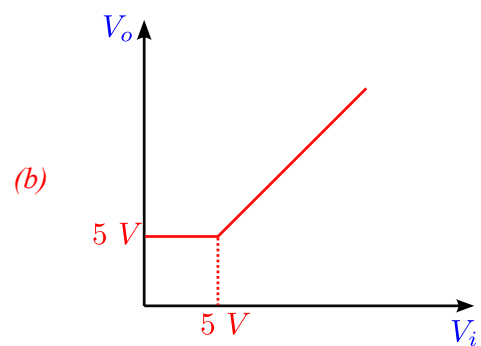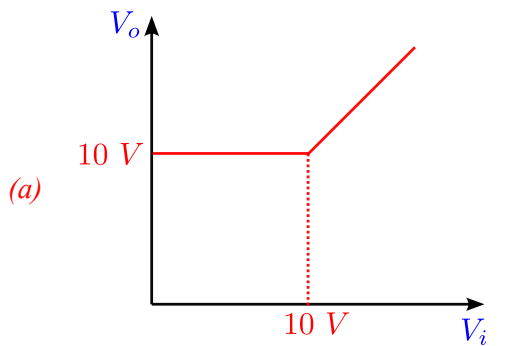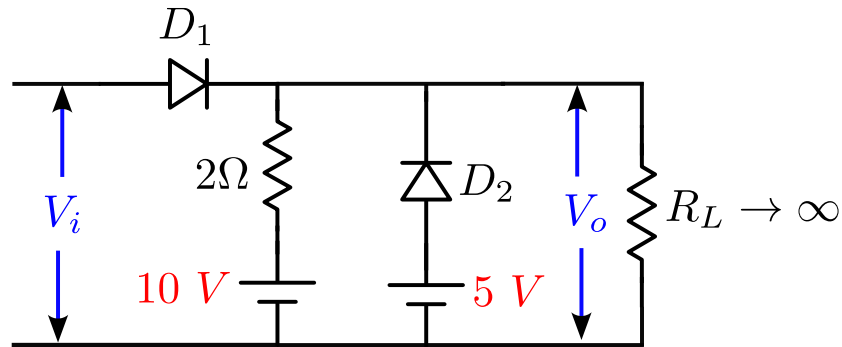Question 10:

Assuming the diodes to be ideal, the transfer characteristics of the circuit will be



Solution: Correct option is (a)

The output voltage  $V_o$  becomes equal to  $V_i$  only when  $V_i > 10\text{ V}$ . Else,  $V_o = 10\text{ V}$ , as there is no path for the current to flow and hence no voltage drop across  $2\Omega$  resistor.